

Energia Fotovoltaica

Parte II - Materiais Fotovoltaicos e Agregações de Células PV

Prof. Tom Overbye, U. of Illinois

Prof. Antonio Simões Costa,
EEL/UFSC

PV Materials




- There are many different materials used for PV cells;
- However the marketplace is dominated by three technologies:
 - *Monocrystalline silicon (mono-si);*
 - *Polycrystalline silicon (p-Si);*
 - *Thin film.*

PV Material Market Share



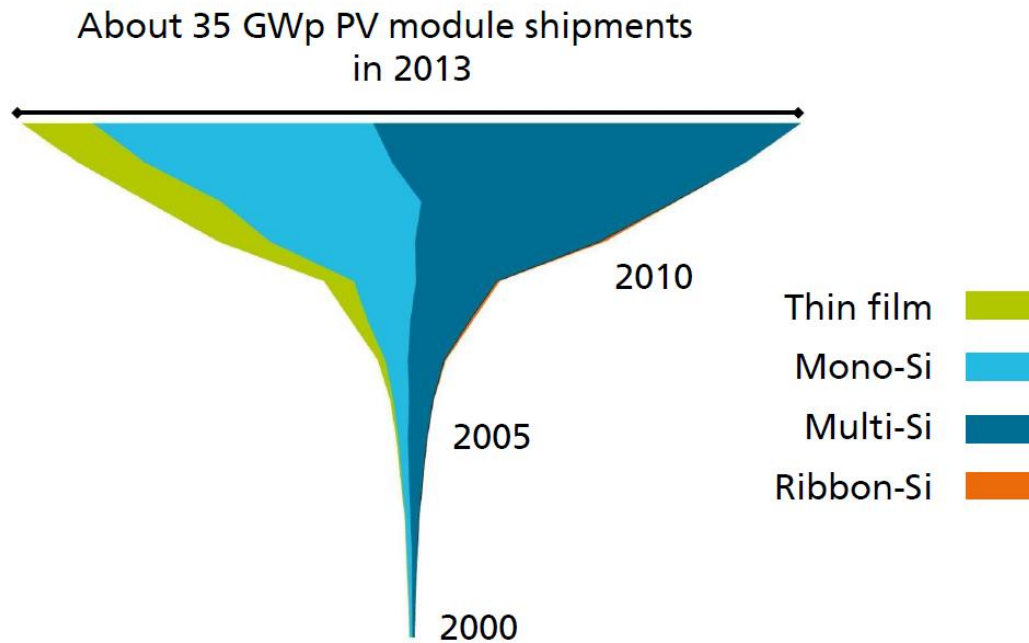Global Annual PV Production by Technology



Note that silicon continues to dominate in market share

Data: Navigant Consulting and IHS; since 2012: estimation from different sources. Graph: PSE AG 2014

Monocrystalline Silicon (mono-si)



- Also called crystalline silicon
- Made out of high grade silicon ingots that are *cylindrical* in shape (Czochralski method)
 - Their edges are cut \Rightarrow sq. cross section, significant waste
 - Have a even coloring and a uniform look
- These panels tend to cost more but have higher efficiency and longer life
 - Example: SunPower E20 series with 20% efficiency



Polycrystalline Silicon (p-Si) or Multi-crystalline Silicon (mc-Si)



- Oldest of the commercial PV panels
- Silicon is melted and poured into square molds
 - Result is square wafers, with no side cuts
- Advantages are that they are less expensive, and result in less waste
- Disadvantage is efficiency is lower (13-16%); more speckled appearance

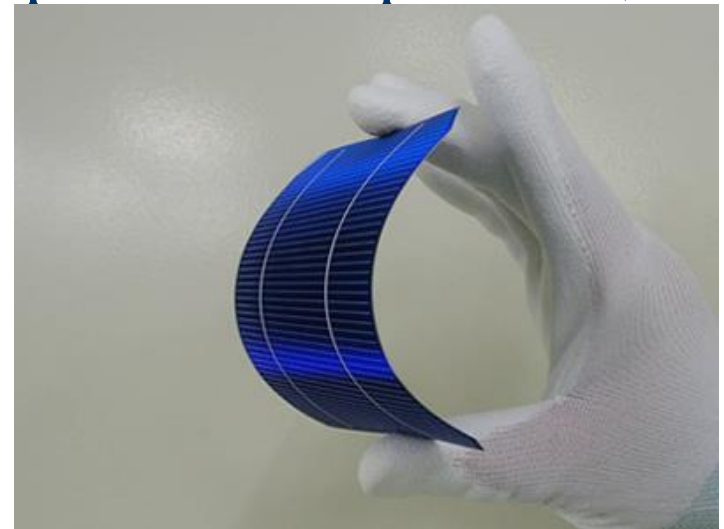


Image: <http://dev.msbs.net/Portals/0/images/PolycrystallineSolarPanel.jpg>


Thin-Film Solar Cells




- Thin-film solar cells are created by depositing one or more layers of material onto glass or metal substrate
 - Examples include amorphous silicon (a-Si), gallium arsenide (GaAs) (arseniato de gálio), cadmium telluride (CdTe), copper indium gallium selenide (CIS) (telureto de cádmio, seleneto de cobre-índio-gálio)
- Advantages are that they are simple to mass produce, have a uniform appearance, and can be flexible
- Disadvantages are they are not very efficient, and may degrade faster



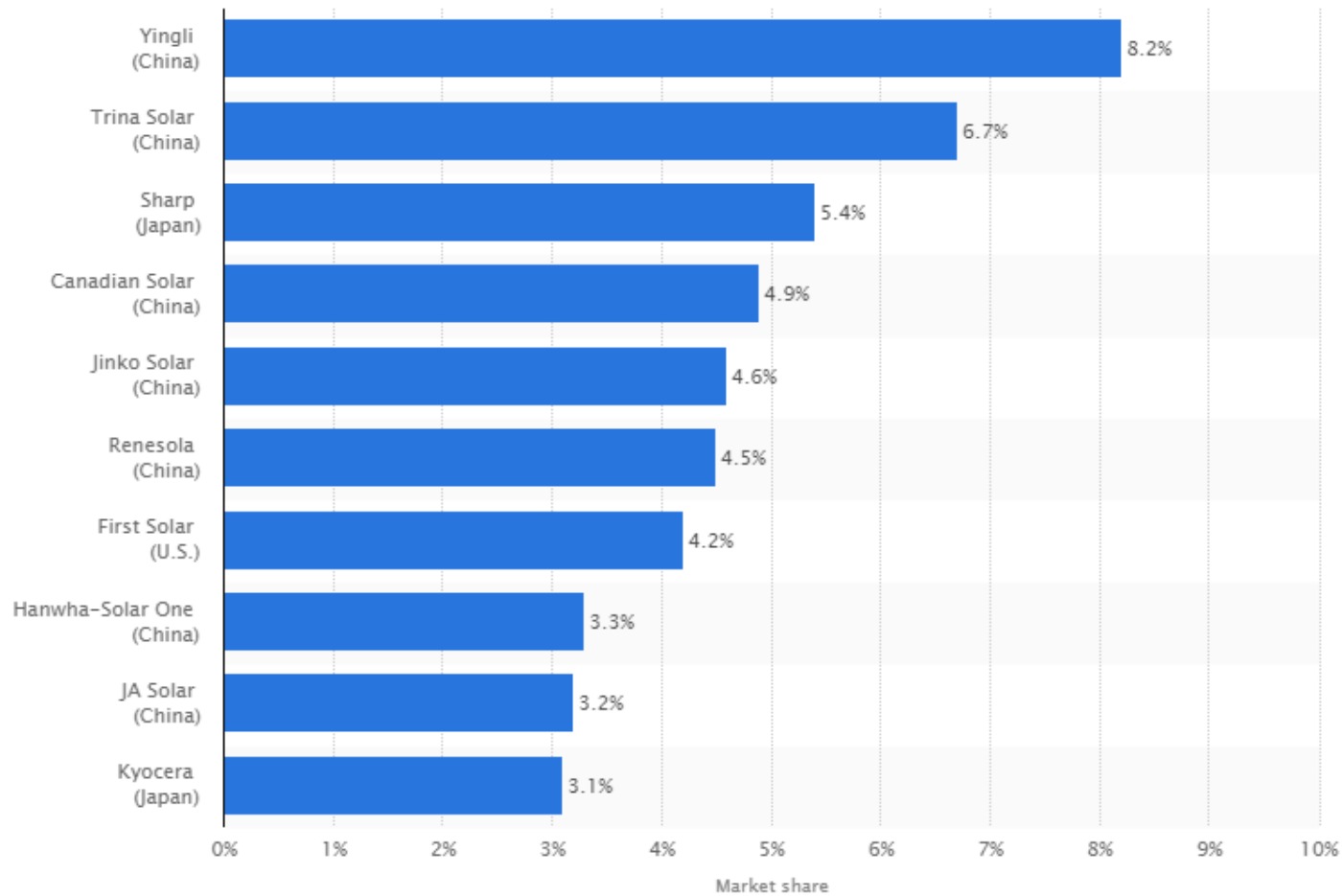Global Market Share PV Manufacturers, 2013




Solar PV Prices Have Recently Dropped

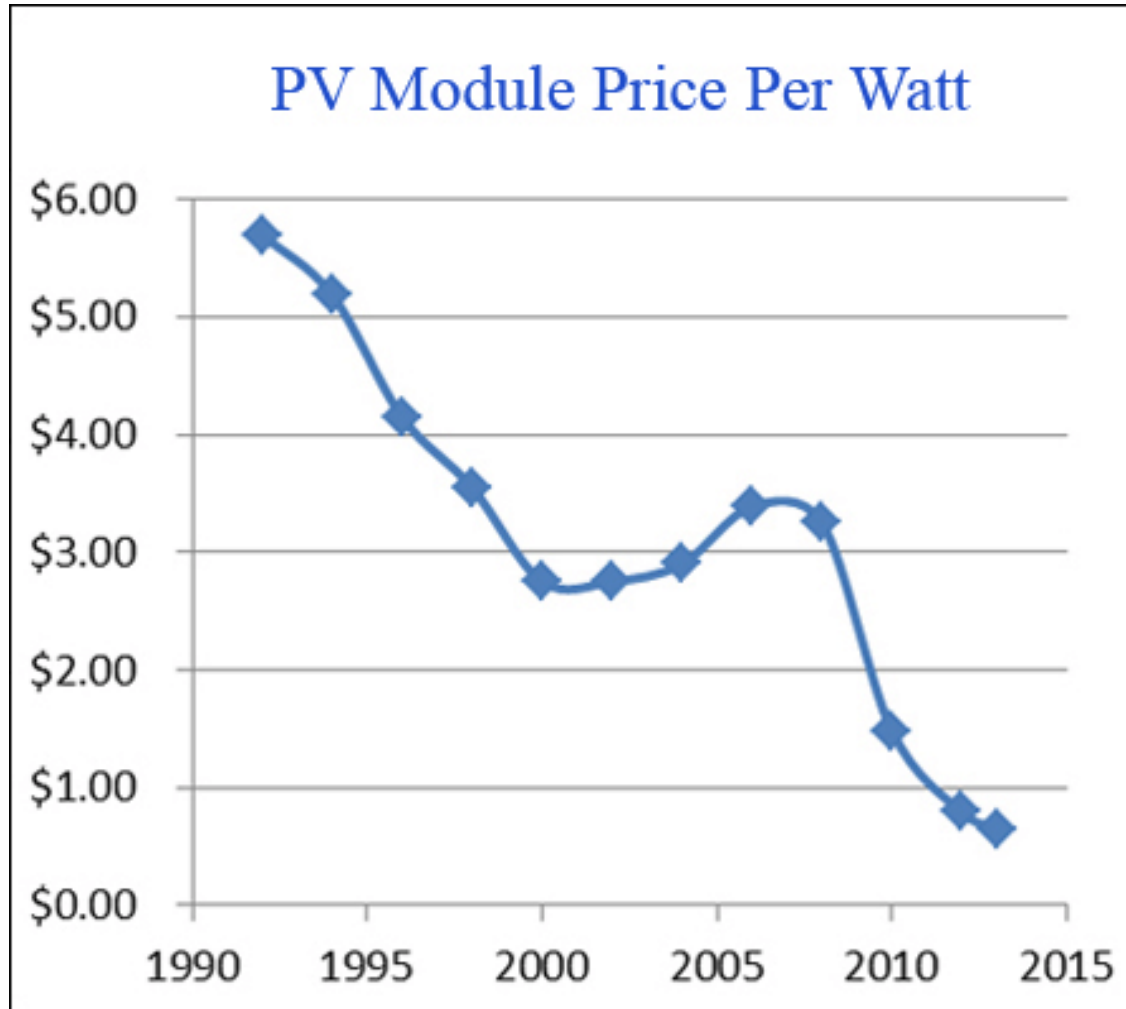

Single Cell Example



Equivalent Circuit:

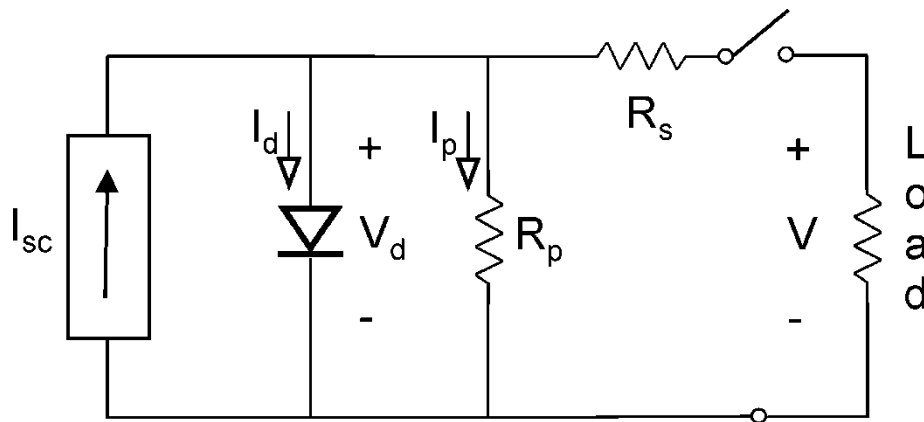

Assume $I_0 = 5 \times 10^{-11}$ A,
 $I_{sc} = 5$ A, $R_p = 5 \Omega$, $R_s = 0.01 \Omega$.
At 25°C what is V_{oc} ?

$$I_{sc} = I_d + \frac{V_d}{5}$$

$$5 = 5 \times 10^{-11} (e^{38.9V_d} - 1) + \frac{V_d}{5}$$

That equation cannot be solved directly, but an iterative solution can be found (guess a V_d and solve with Newton's method). Guess $V_d = 0.65$, next iteration is 0.6504.

Single Cell Example Continued: V-I Curve



- To generate the output V-I Curve

- Pick a value of V_d
- Solve for I_d
- Solve for I_p
- $I = I_{sc} - I_d - I_p$
- $V = V_d - R_s * I$

Assume $V_d = 0.64$, $I_{sc} = 5A$


$$I_d = 5 \times 10^{-11} (e^{38.9V_d} - 1) = 3.245$$

$$I_p = \frac{0.64}{5} = 0.128$$

$$I = 5 - 3.245 - 0.128 = 1.627$$

$$V = 0.64 - 0.01 \times 1.558 = 0.624$$

Equivalent Circuit:

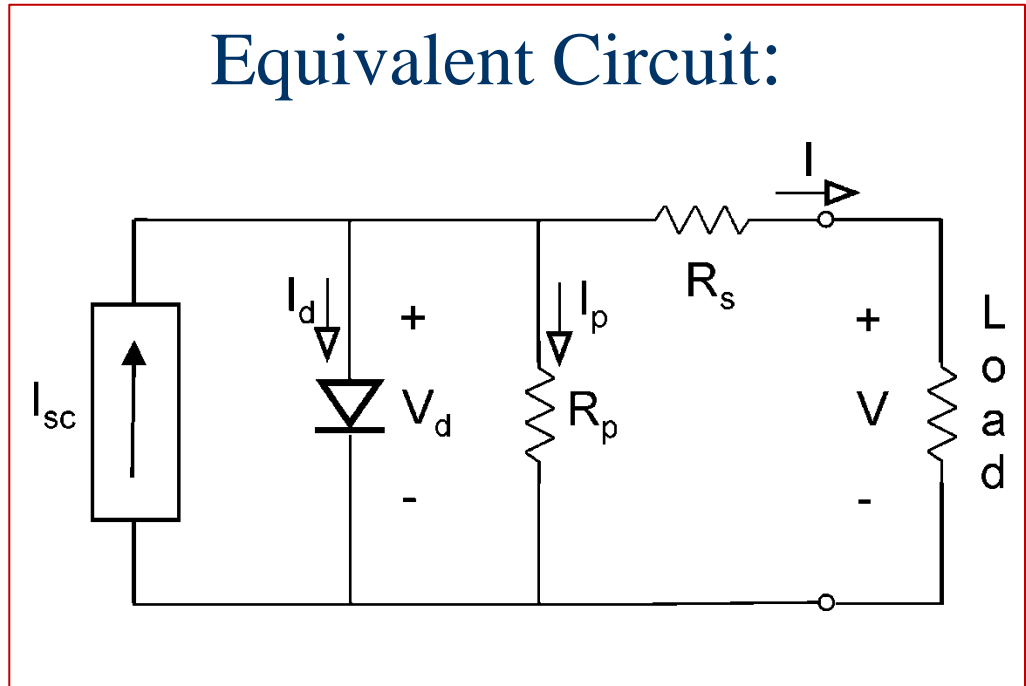


This is one point on the curve

Cells as Building Blocks



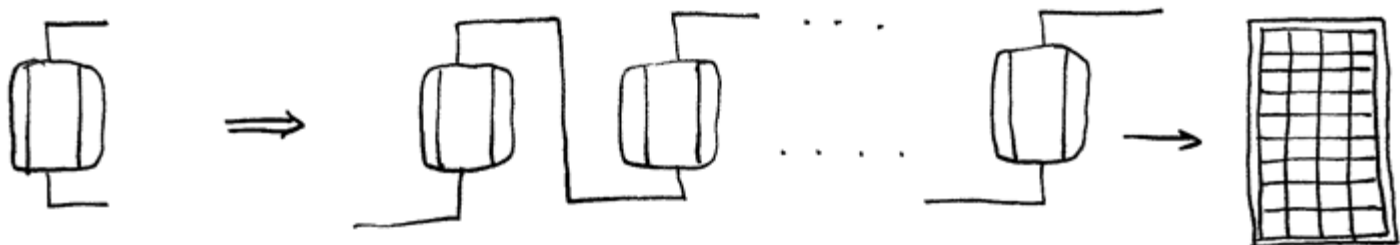- The *open circuit voltage* of a solar cell is $\cong 0.6$ V and $\cong 0.5$ V when the cell is loaded
- Since 0.5 V is rather low for power applications, it is rare that we use one individual cell
- Instead, we use *modules*, which consist of a bunch of individual cells in series, encased in a tough, weather-resistant package
- The modules are commonly connected into *arrays*




Cells to Modules to Arrays



Cell



Module

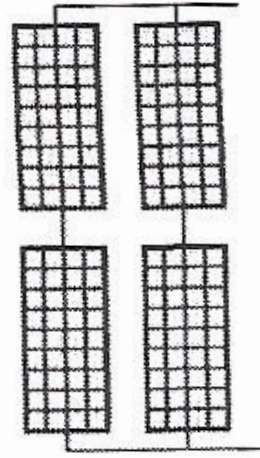

Array

Rain, hail,
ice, snow

Local failures,
shadows


Heat, humidity,
corrosive gases

Modules – A **12V module** has 36 cells wired in series,
each cell ~ 0.5 V

72-cell modules are also common (usually 24 V)

Arrays – combination of modules connected in series
and/or in parallel

Module with Simple Cell Model

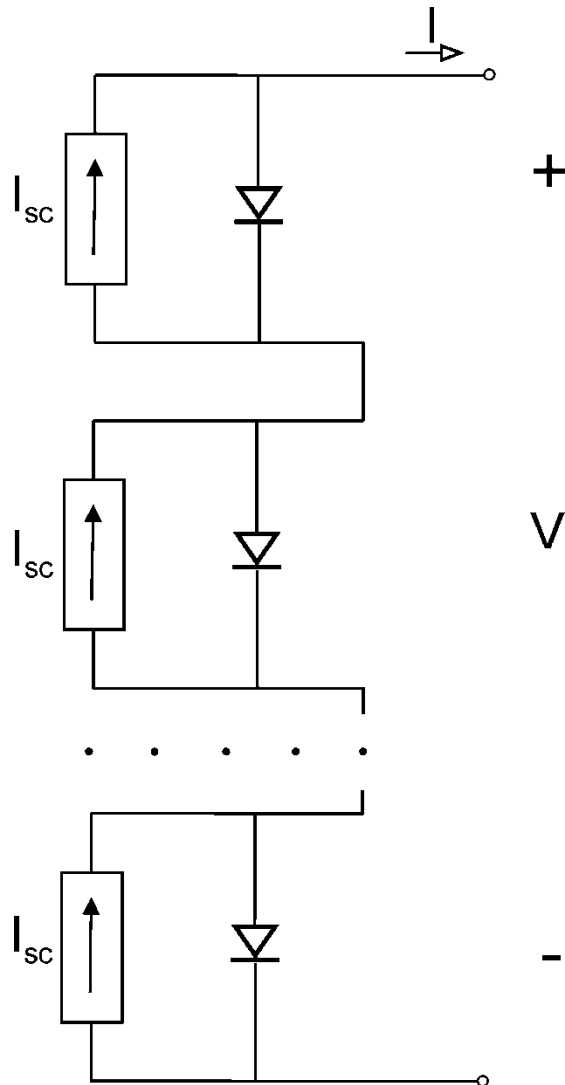

Using the *simplest model* of a cell:

$$V = V_1 + V_2 + \dots + V_n = nV_d$$

$$I = I_{SC} - I_d$$


For one cell (in the sun):

$$I = I_{SC} - I_0(e^{qV_d/kT} - 1)$$

$$e^{qV_d/kT} = \frac{I_{SC} - I}{I_0} + 1$$

$$V_d = \frac{kT}{q} \ln \left(\frac{I_{SC} - I + I_0}{I_0} \right)$$

Module with Simple Cell Model

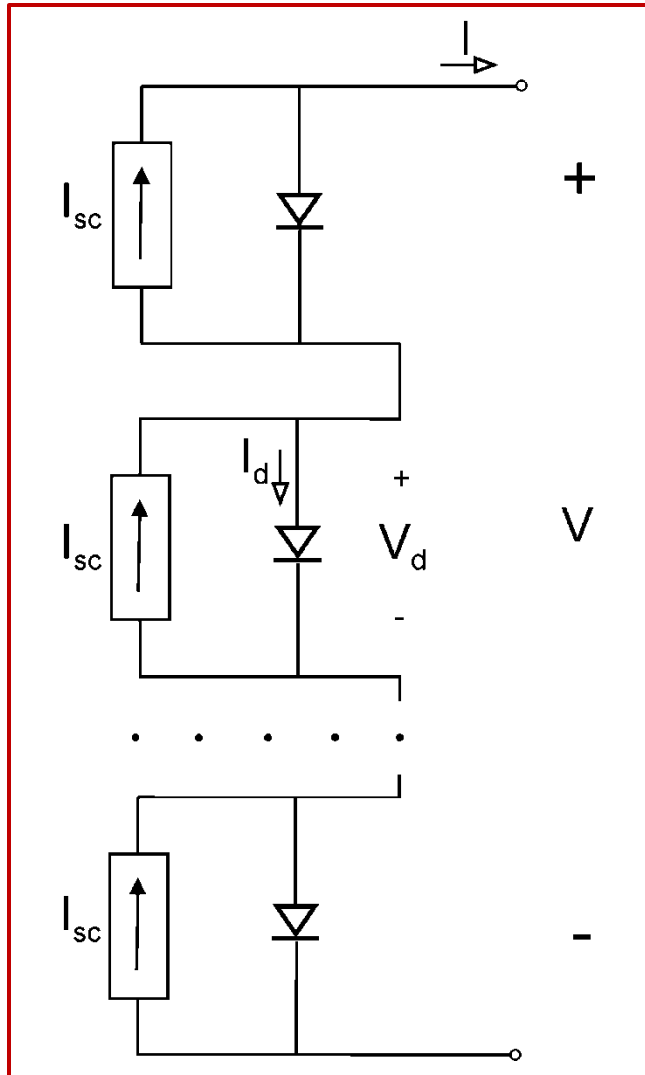


For the entire module


$$V = n \cdot \frac{kT}{q} \ln \left(\frac{I_{sc} - I + I_0}{I_0} \right)$$

$$I = I_{sc} - I_0 (e^{qV/nkT} - 1)$$
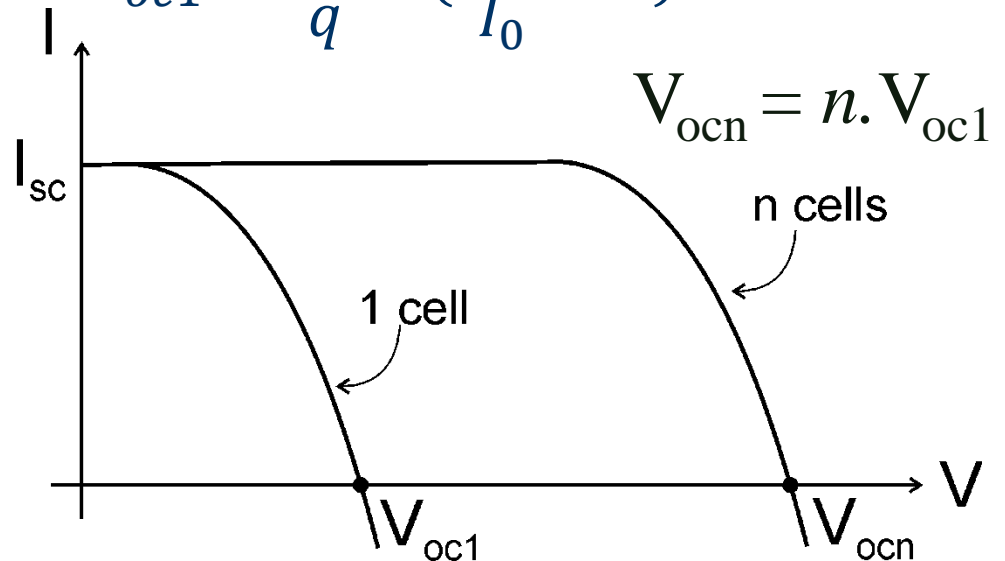
$$V_{oc1} = \frac{kT}{q} \ln \left(\frac{I_{sc}}{I_0} + 1 \right)$$



Module with Parallel-Only Cell Model

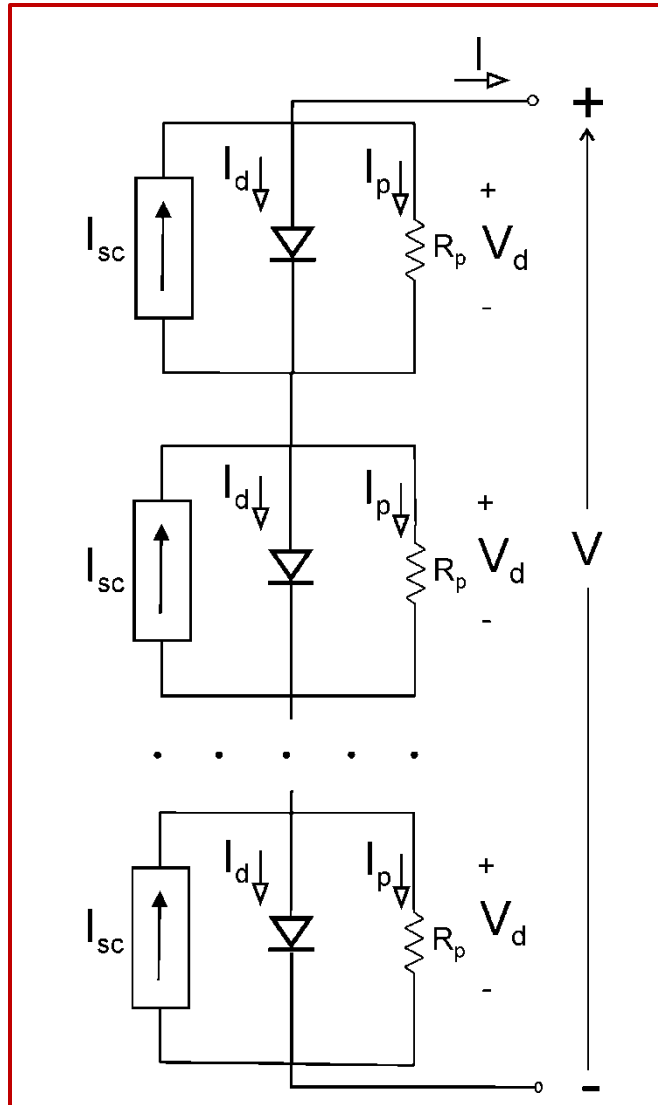

For one cell (in the sun)

$$V = nV_d$$

$$I_d = I_{SC} - I - \frac{V_d}{R_p}$$

$$V_d = \frac{kT}{q} \ln \left(\frac{I_d}{I_0} + 1 \right)$$

For the entire module

$$V = n \cdot \frac{kT}{q} \ln \left(\frac{I_{SC} - I - V / (nR_p)}{I_0} + 1 \right)$$

$$I = I_{SC} - I_0 (e^{qV/nkT} - 1) - \frac{V}{R_p n}$$

Module Example




Assume 36 identical cells in series with $I_0 = 5 \times 10^{-11}$ A, $I_{sc} = 5$ A, $R_p = 5 \Omega$, $R_s = 0 \Omega$. At 25°C what is V_{oc} ?

$$I_{sc} = I_d + \frac{V}{5 \times 36}$$


$$5 = 5 \times 10^{-11} (e^{38.9V/36} - 1) + \frac{V}{5 \times 36}$$

That equation again cannot be solved directly, but an iterative solution can be found: $V = 23.41$ V

Module with General Cell Model

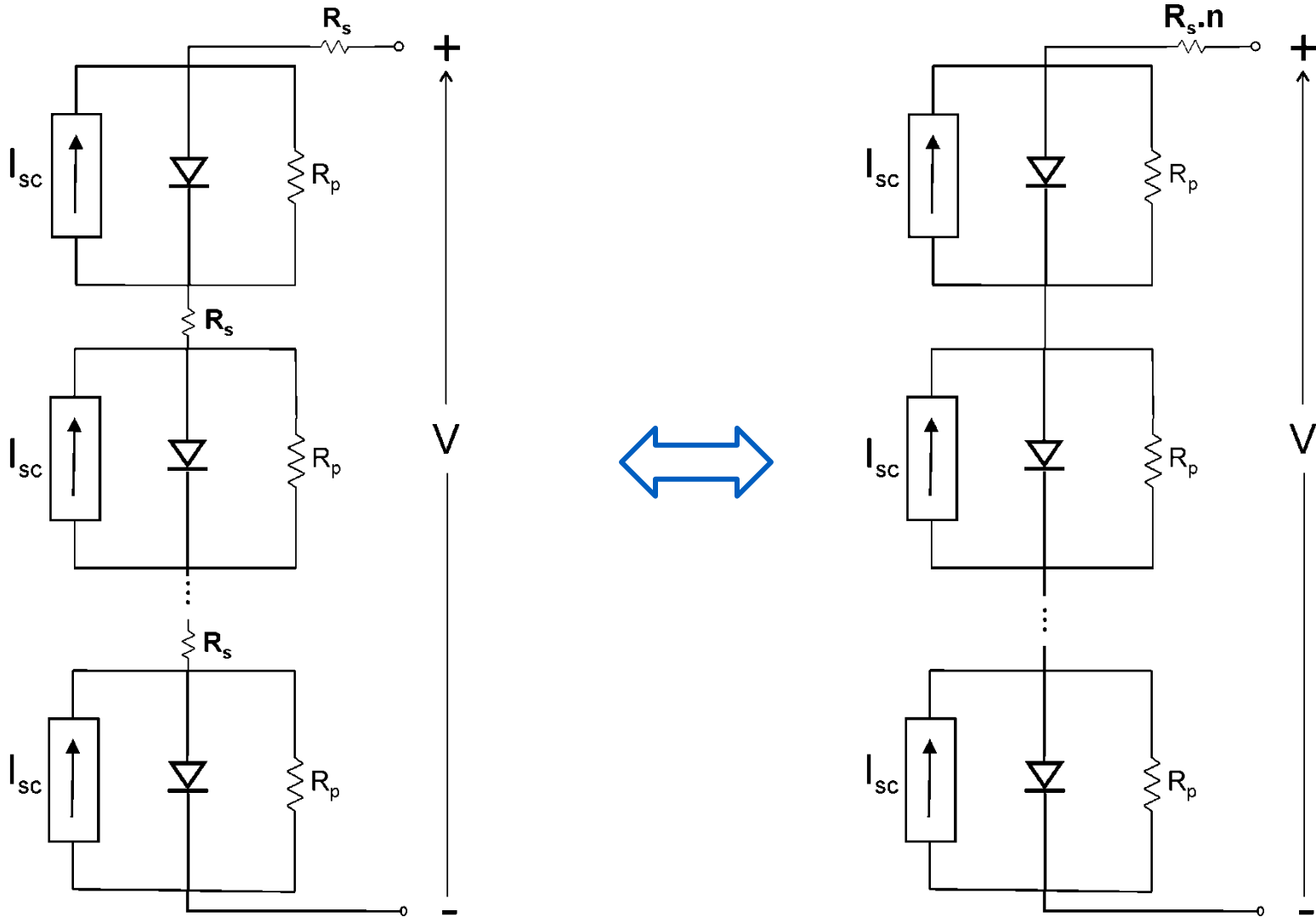

Module with General Cell Model

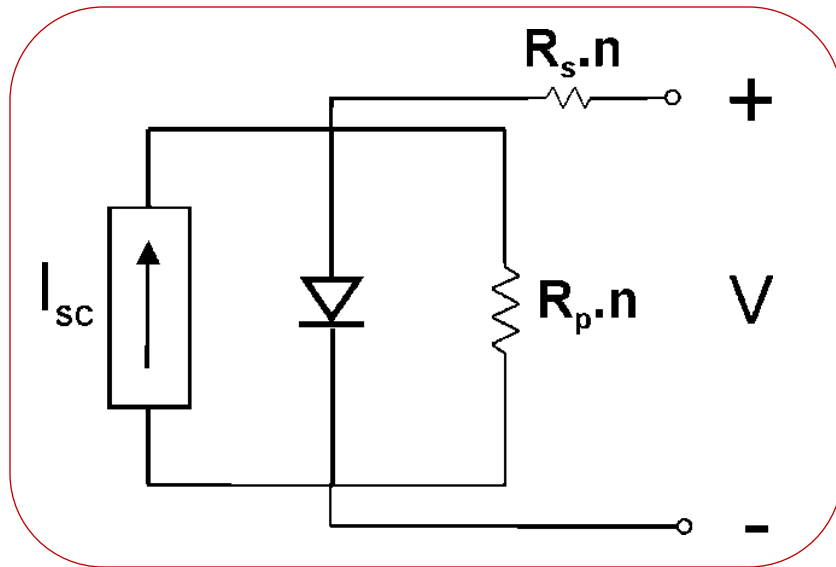

For the entire module:

$$V = n(V_d - IR_S)$$

$$V + nIR_S = nV_d$$

Writing the equations in terms of V and I:

$$I = I_{SC} - I_0 \left(e^{q(V + I \cdot nR_S)/nkT} - 1 \right) - \frac{V + I \cdot nR_S}{R_p n}$$

Module Example Continued: V-I Curve



- Generating the V-I Curve again requires picking a V_d
 - Pick a value of V_d
 - Solve for I_d
 - Solve of I_p
 - $I = I_{sc} - I_d - I_p$
 - $V = n(V_d - R_s * I)$

Assume $V_d = 0.64$, $I_{sc} = 5A$

$$I_d = 5 \times 10^{-11} (e^{38.9V_d} - 1) = 3.245$$

$$I_p = \frac{0.64}{5} = 0.128$$

$$I = 5 - 3.245 - 0.128 = 1.627$$

$$V = 36 \times (0.64 - 0.01 \times 1.627) = 22.45$$

Modules in Parallel



- Modules in parallel increase the current

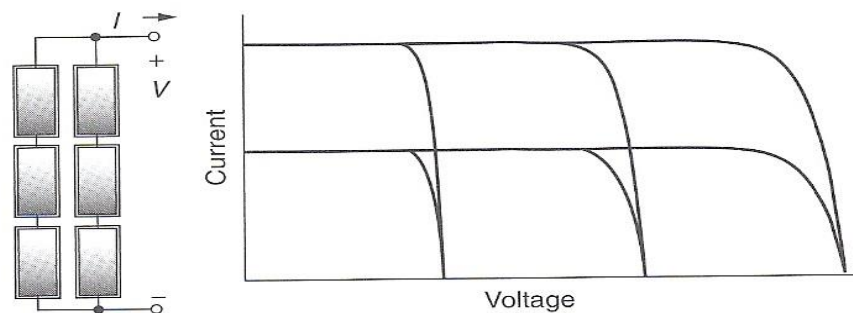


FIGURE 5.37 The total I - V curve of an array consisting of two strings of three modules each.

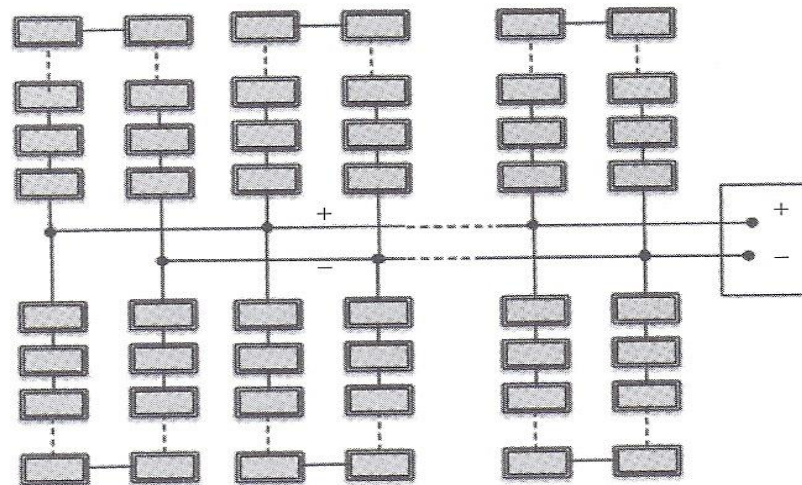


FIGURE 5.38 Multiple strings in parallel for large power arrays.

Standard Test Conditions



- PV modules are tested under standard conditions of 1 kW/m^2 and a cell temperature of 25°C .
- Rating is the power at the maximum power point (MPP); fill factor is ratio of MPP to $V_{oc} \times I_{sc}$


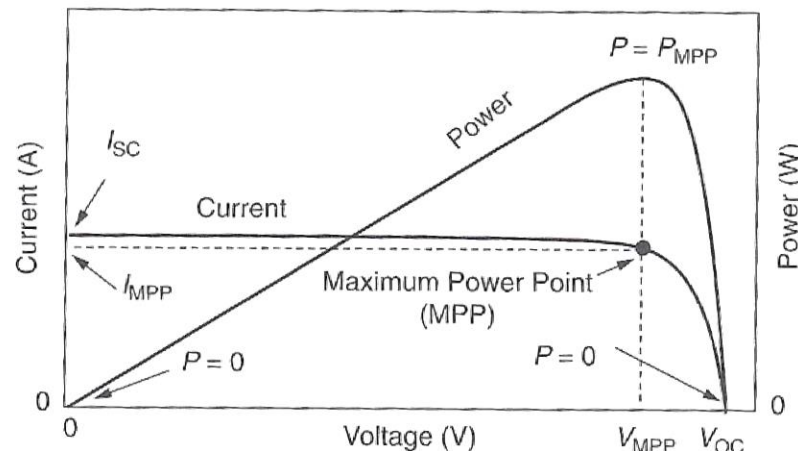


FIGURE 5.40 The I - V curve and power output for a PV module. If drawn under standard test conditions, the MPP identifies the rated voltage V_R , current I_R , and power P_R for the module.

Impact of Temperature and Insolation

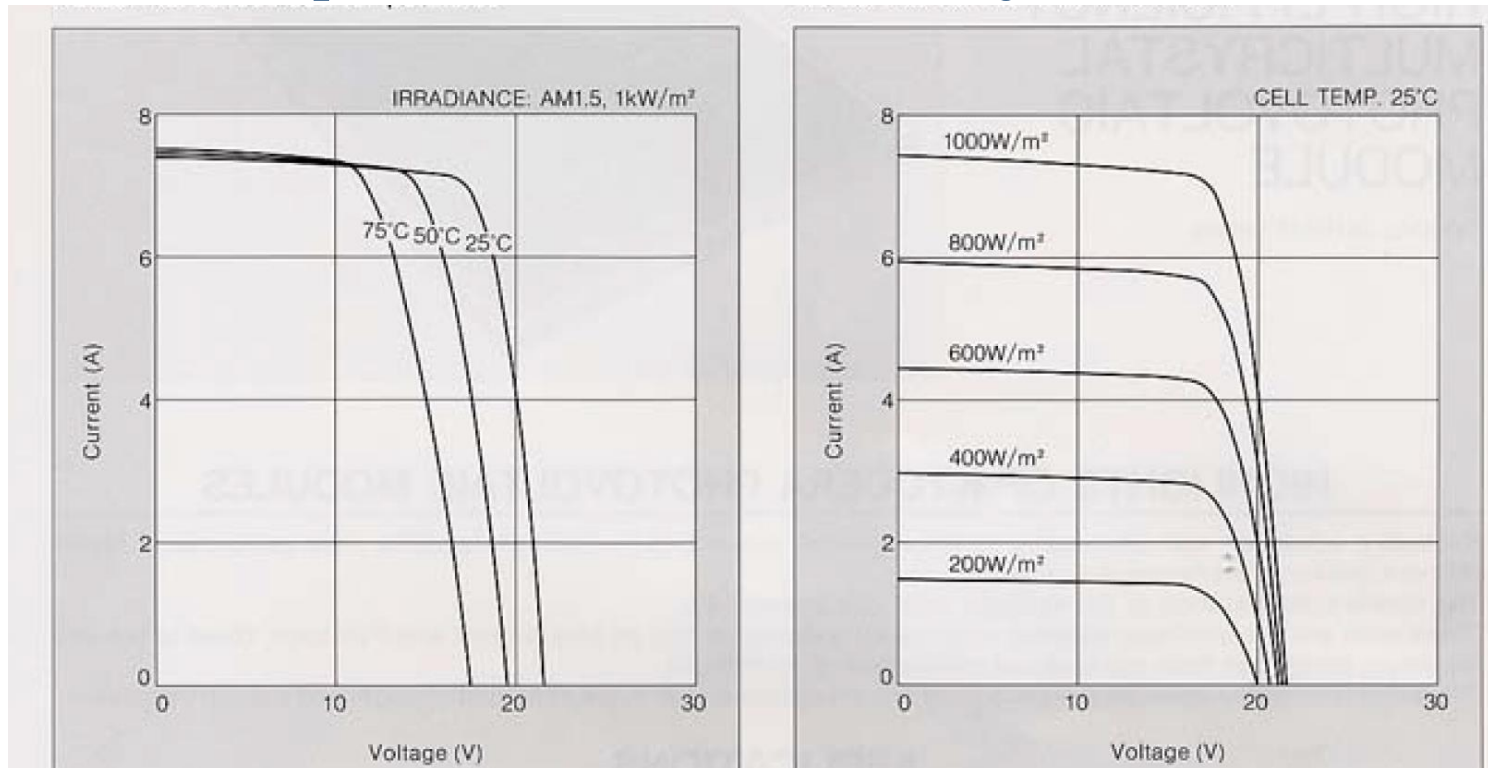

- Cell output is sensitive to both temperature and insolation (might be on the order of 0.3% per degree C
 - Temperature for cell, which might be well above ambient!




Figures are for a Kyocera KC120 module using mc-Si

Impact of Shading






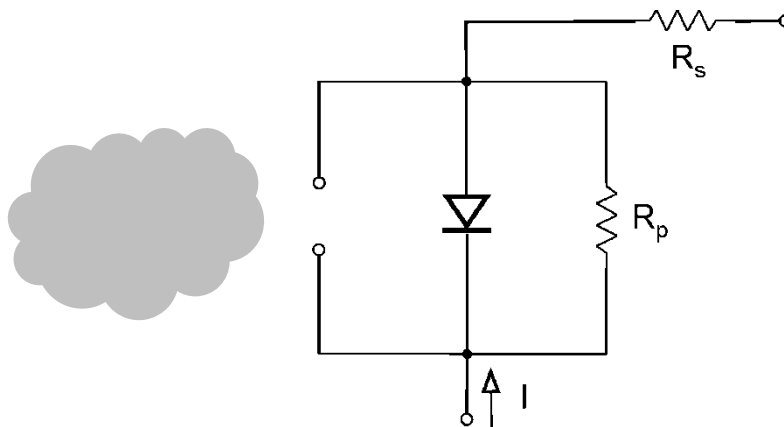- The output of a PV module can be severely reduced (>50%) if even a small portion is shaded
- A single cell in a long string of cells that is shaded limits the current of the entire string, since cells in series must carry the same current
- Essentially, a PV cell in the shade acts like a resistor instead of a current source in parallel with a diode:



- I_{SC} is zero;
- Diode is reverse biased (off);
- I flows through R_p , R_s

Shading Impact on Output Voltage

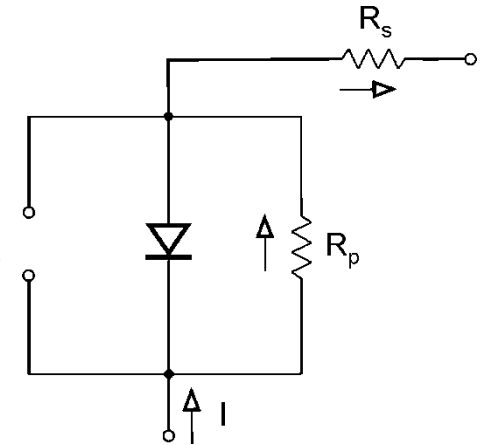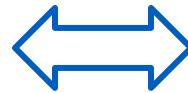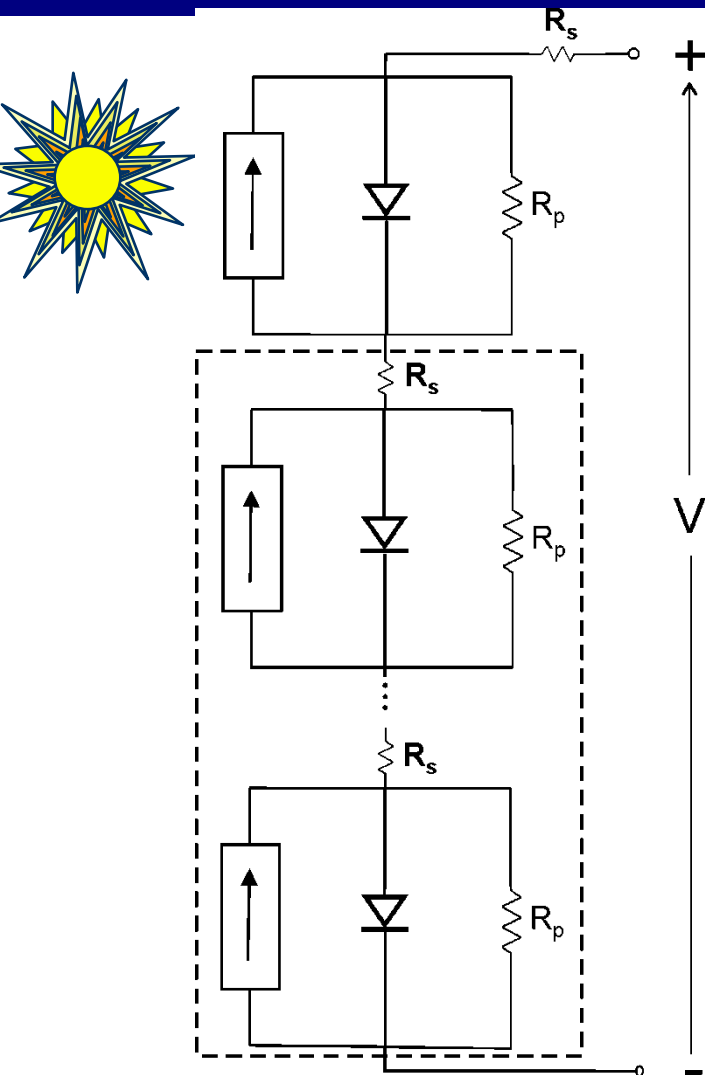

Voltage across n non-shaded cells:

$$V_n = nV_i = V$$


or $n-1$ non-shaded cells:

$$V_{n-1} = (n-1)V_i = \frac{(n-1)}{n}V$$

Voltage Drop due to Shading



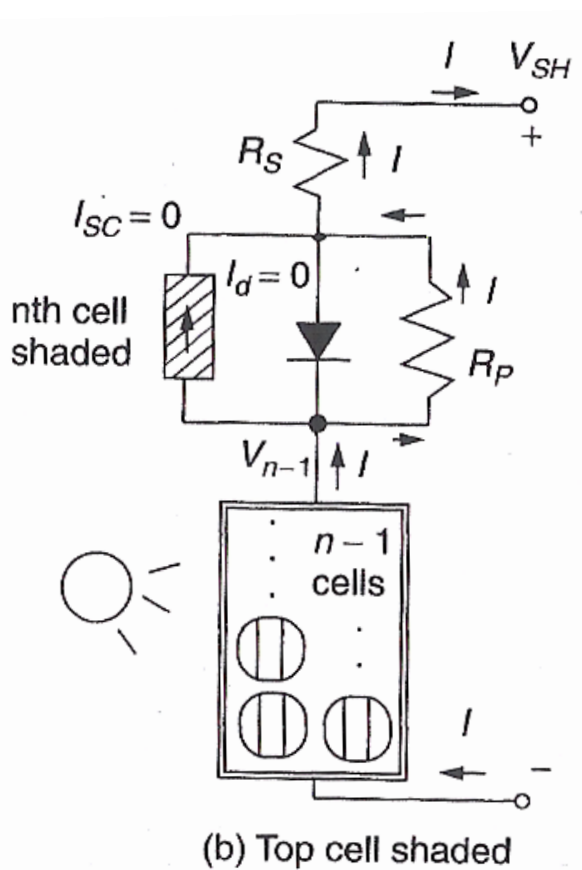
- Drop in output voltage due to shading = a loss in what it would produce (V/n) plus a resistive drop (IR)



$$V_{SH} = \left(\frac{n-1}{n} \right) V - I (R_S + R_P)$$

$$\Delta V = \frac{V}{n} + I (R_S + R_P)$$

R_p is $\gg R_s$!

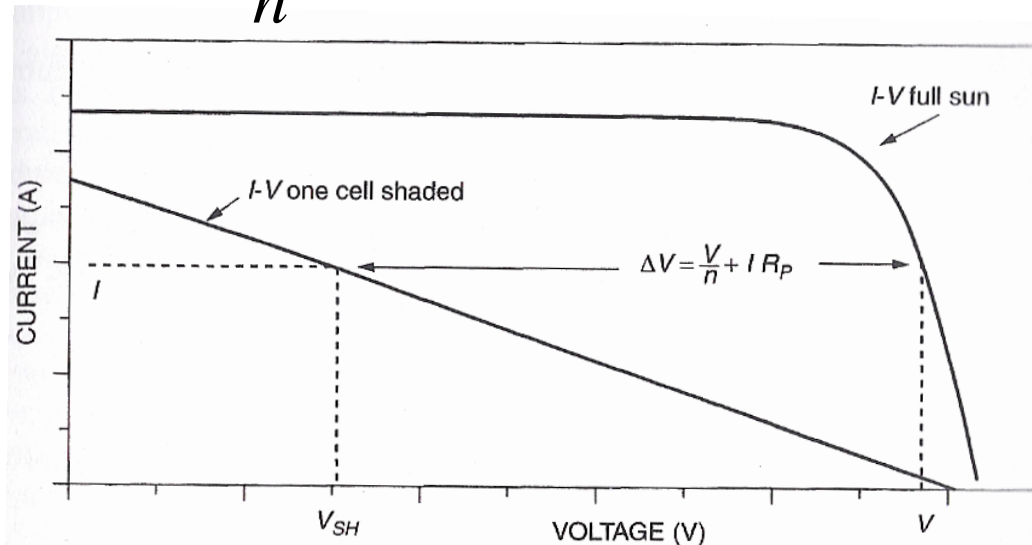

Shading Example



- Assume a 36 cell PV module with per cell $R_p = 6.6 \Omega$. In full sun the output current is 2.14 A and the output voltage is 19.41 V. $P_{out} = 41.5$ W. If one cell is shaded, and the current stays the same, what is the new output voltage and power?

$$\Delta V = \frac{V}{n} + IR_p$$

$$\Delta V = \frac{19.41}{36} + 2.14 \times 6.6 = 14.66 \text{ V}$$

$$V_{new} = 19.41 - 14.66 = 4.75 \text{ V}$$


$$P_{new} = 4.75 \times 2.14 = 10.2 \text{ W}$$

With one cell shaded the output is < 25% of original! Lost power is dissipated as heat in the shaded cell.

Shading Mitigation



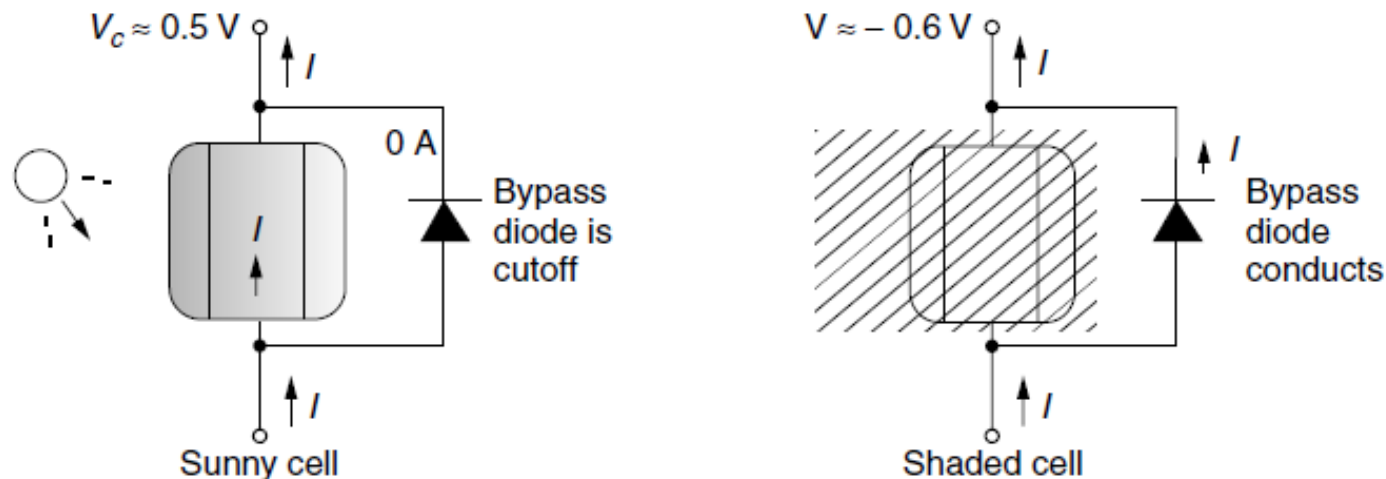
- Solution - bypass diodes to bypass the shaded cell
- Instead of an $I(R_p + R_s)$ voltage drop across the resistors, only a fixed voltage drop due to the diode, about 0.6 V (or even smaller with special diodes)
- No effect during normal operation



Bypass Diodes





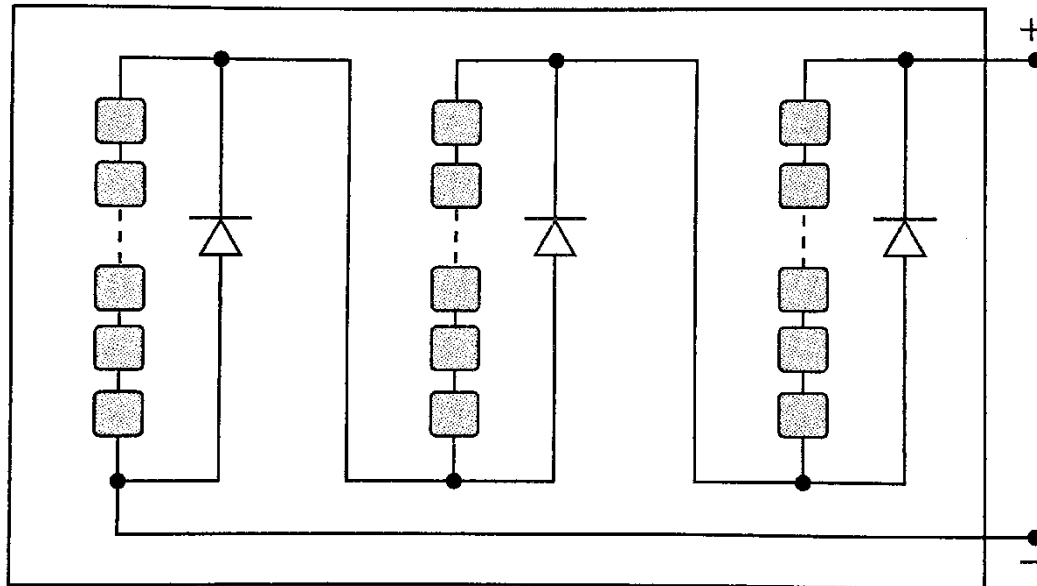- It may be difficult to add one bypass diode to each cell;
- Instead, add the diode to a group of cells such as a module or string:



For example, with three diodes for a module the voltage would drop by about $1/3$

Bypass Diode Impact on Module

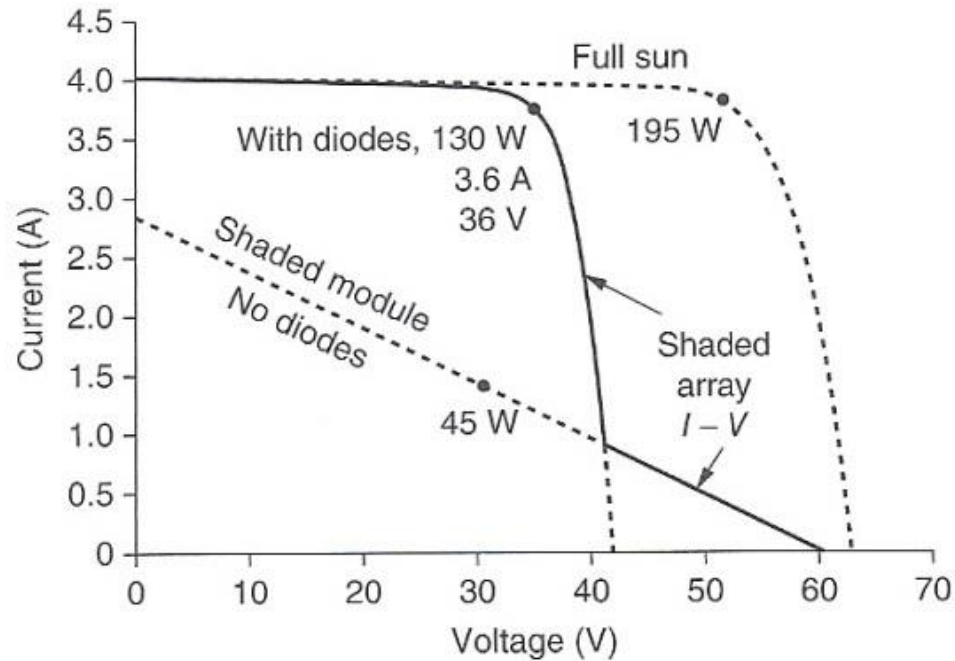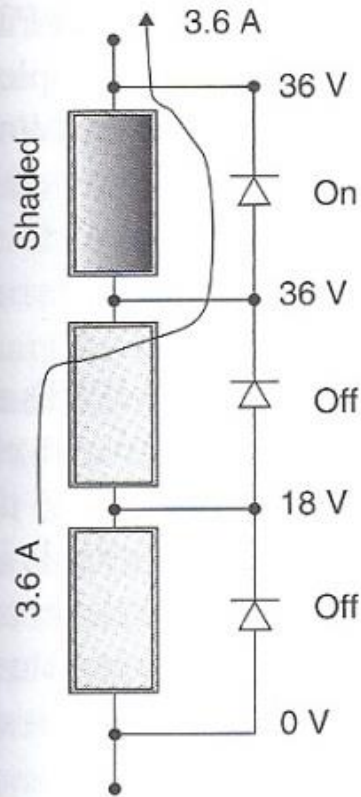

Bypass diodes also prevent overheating of shaded cells

FIGURE 5.50 Showing the ability of bypass diodes to mitigate shading problems in a string of modules.