

Energy Storage: Batteries

Part II: Equivalent Circuits and Connection to Main Grid

Prof. Antonio Simões Costa
UFSC

Prof. Hrvoje Pandžić
Univ. of Zagreb

Equivalent Circuit models for Batteries

- ▶ Batteries are often modeled as equivalent circuit diagrams based on the Thevenin's theorem;
- ▶ Those models are available under three different forms, namely:
 - ▶ The **internal resistance** model (**IR**);
 - ▶ The **one time constant** model (**OTC**), and
 - ▶ The **two time constants** model (**TTC**).


The Internal Resistance Model

- ▶ The model consists of a voltage source, E_b , and an internal resistor, R_i , where

$$E_b = f(\text{SoC}) \quad R_i = f(I_{bat}, \text{SoC}, T)$$

- ▶ E_b is the open circ. voltage, due to energy stored in the batt;
- ▶ R_i represents the losses, and is invers. proport'l to the SoC (when batt is discharging, R_i is increasing);
- ▶ Circuit equation:

$$V_{bat}(t) = E_b(t) + I_{bat}(t) R_i$$

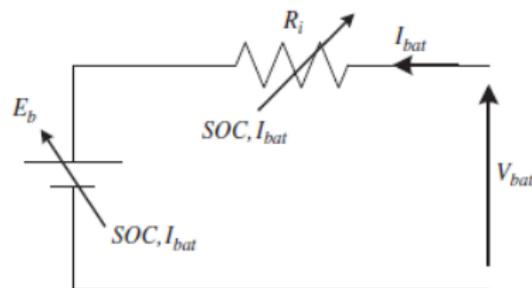

Example: losses and low charging rates

A 100 Ah, 12 V batt with a voltage of 12.5 V (at its current SoC) is charged at C/5 rate, during which time the applied voltage is 13.2 V. Using the IR model:

- Estimate R_i ;
- What fraction of the input power is lost in R_i ?
- If charging is done at C/20 rate, what fraction of the input power would be lost due to R_i ?

Solution (1/2)


a) Estimation of R_i :

At C/5:

$$I_{bat} = \frac{100 \text{ Ah}}{5 \text{ h}} = 20 \text{ A}$$

$$R_i = \frac{V_{bat} - E_b}{I_{bat}} = \frac{13.2 - 12.5}{20}$$

$$R_i = 0.035 \Omega$$

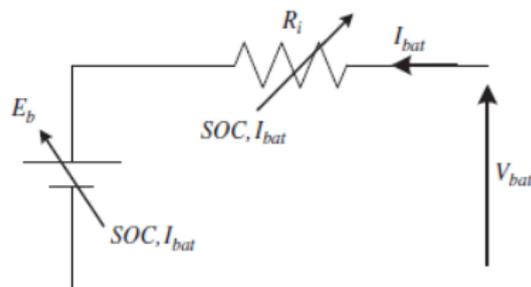

b) Fraction of the input power lost in R_i :

$$\frac{\text{Loss in } R_i}{\text{Input Power}} = \frac{I_{bat}^2 R_i}{V_{bat} I_{bat}} = \frac{(20)^2 \times 0.035}{13.2 \times 20} = 0.053 = 5.3\%$$

Solution (2/2)

c) Fraction of the input power lost in R_i at $C/20$:

At $C/20$:

$$I_{bat} = \frac{100 \text{ Ah}}{20 \text{ h}} = 5 \text{ A}$$

The input power to drive 5 A through $R_i = 0.035 \Omega$ is:


$$V_{bat} = E_b + I_{bat} R_i = 12.5 + 5 \times 0.035 = 12.68 \text{ V}$$

So at the $(C/20) = 5 \text{ A}$ rate, the loss are now only

$$\frac{\text{Loss in } R_i}{\text{Input Power}} = \frac{I_{bat}^2 R_i}{V_{bat} I_{bat}} = \frac{(5)^2 \times 0.035}{12.68 \times 5} = 0.014 = 1.4\%$$


Limitations of the IR Model and Real Battery Curves

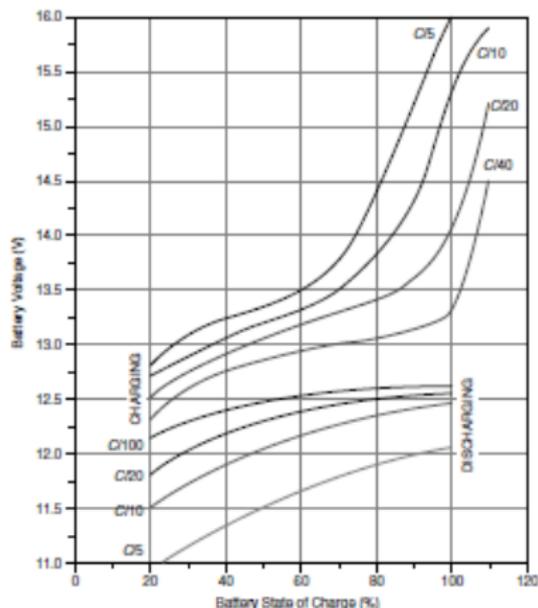- ▶ The *IR* model is useful, but complicated by the fact that both E_b and R_i depend on the SoC, temp, and batt history;
- ▶ The figure show realistic values of E_b for different charging/discharging rates as a function of SoC;
- ▶ Curves are for 12 V lead-acid batteries.




Lead-Acid batteries: practical aspects

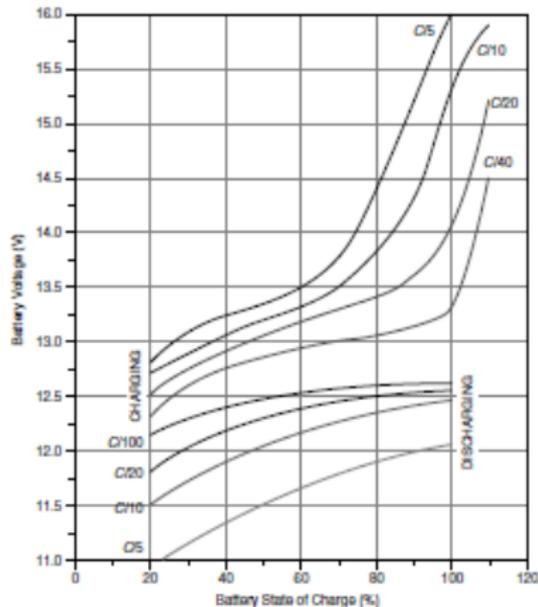- ▶ **Charging:** sudden rise of cell voltage around 14 V level \Rightarrow poor charging efficiency + gassing;
- ▶ Water removed from batt has to be replaced or plates will be damaged;
- ▶ **VRLA batts** reduce gas emission by over 95%;
- ▶ **Charge controllers** slow charging rates and minimize losses+gassing.



The One Time Constant Model (1/2)

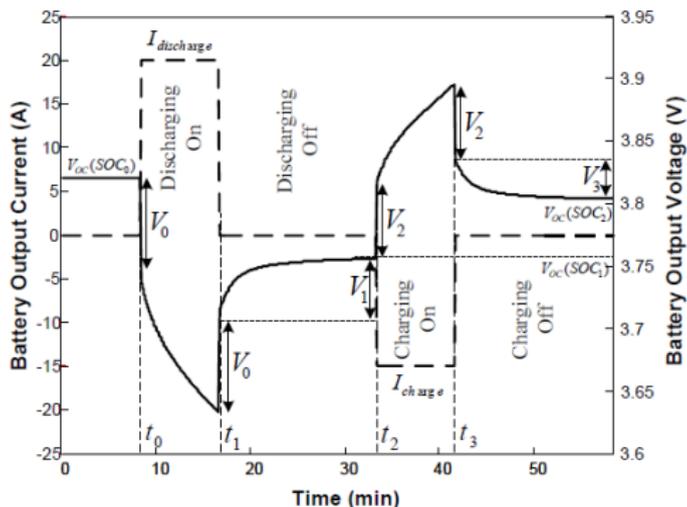- ▶ The IR model does not represent the transient behavior of batteries, and in particular of Li-ion cells;
- ▶ Li-ion cell curves for batt V and I during charging/discharging cycles (notice they are typical of RC circuits):




The One Time Constant Model (2/2)

- ▶ The OTC model adds a parallel RC network in series with the internal resistance:
 - ▶ R_0 : internal resistance;
 - ▶ R_1, C_1 : parameters of RC network.
 - ▶ E_m : open circuit voltage

- ▶ Mathematical model:

$$\dot{V}_1 = -\frac{1}{R_1 C_1} V_1 + \frac{1}{C_1} I_{dc}$$

$$V_{dc} = E_m - V_1 + R_0 I_{dc}$$

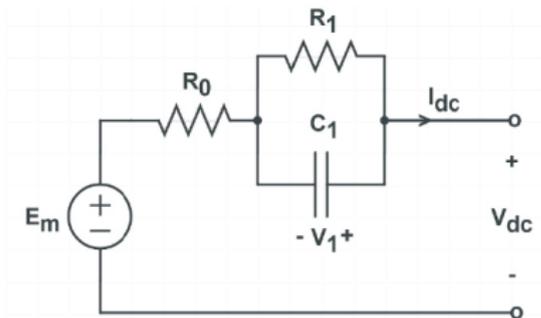


The Two Time Constants Model (1/2)

- ▶ The TTC model is aimed at improving the dynamic behavior and flexibility of the OTC model;
- ▶ An extra RC network is added in series with the OTC circuit;
- ▶ **Mathematical model:**

$$\dot{V}_1 = -\frac{1}{R_1 C_1} V_1 + \frac{1}{C_1} I_{dc}$$

$$\dot{V}_2 = -\frac{2}{R_2 C_2} V_2 + \frac{1}{C_2} I_{dc}$$
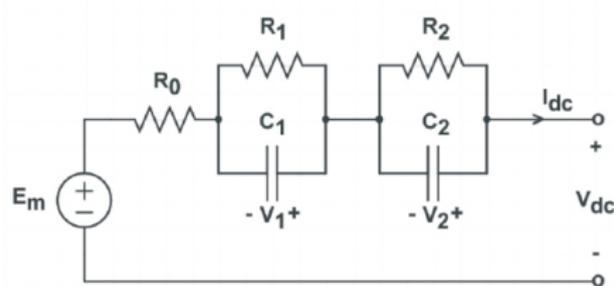
$$V_{dc} = E_m - V_1 - V_2 + R_0 I_{dc}$$



Final Remarks on Battery Equivalent Circuits

- ▶ The parameters of the two improved models (OTC and TTC) are estimated through laboratory experiments and the use of a nonlinear least squares algorithm (nonlinear data fitting);

Final Remarks on Battery Equivalent Circuits


- ▶ The parameters of the two improved models (OTC and TTC) are estimated through laboratory experiments and the use of a nonlinear least squares algorithm (nonlinear data fitting);
- ▶ It is generally considered that the OTC model approximately describes the dynamic characteristics of a battery, but the TTC model is more accurate for Li-ion batteries and should be preferred;

Final Remarks on Battery Equivalent Circuits

- ▶ The parameters of the two improved models (OTC and TTC) are estimated through laboratory experiments and the use of a nonlinear least squares algorithm (nonlinear data fitting);
- ▶ It is generally considered that the OTC model approximately describes the dynamic characteristics of a battery, but the TTC model is more accurate for Li-ion batteries and should be preferred;
- ▶ Those models can be used to develop enhanced methods for SOC estimation.

Connection of Battery Storage Energy Systems to the Grid


- ▶ There are different means to connect a BESS to an AC grid;
- ▶ A possible arrangement for such connection is based on a 12-pulse converter equipped with a controller:

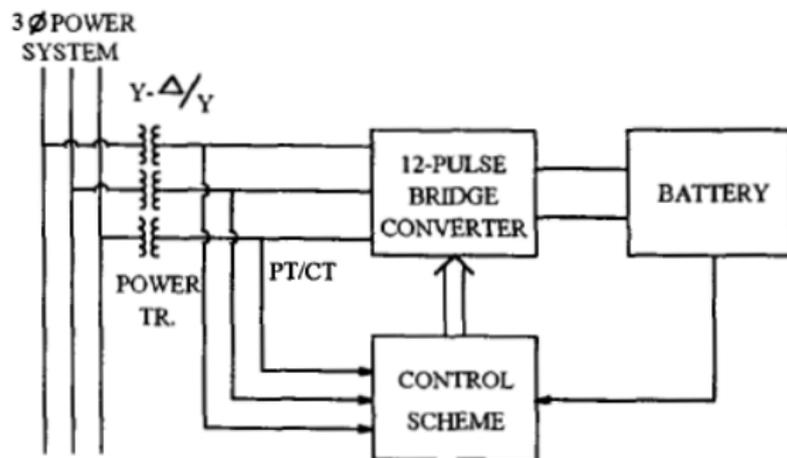


The 12-pulse converter: topology (1/2)

- ▶ It is formed by associating two 6-pulse converter bridges in parallel, each of them connected to the grid by a distinct transformer;
- ▶ In order to reduce the input harmonics of the 3-phase rectifiers, phase-shifting transformer circuits are used:
 - ▶ One of the 6-pulse rectifier bridge is connected through a Y-Y transformer;
 - ▶ The other 6-pulse rectifier bridge is connected through a Y- Δ transformer.
- ▶ Since Δ -Y transformers cause a 30° phase shift between primary and secondary line-to-line voltages, [this scheme eliminates low-order harmonics, such as the fifth and seventh.](#)

The 12-pulse converter: topology (2/2)

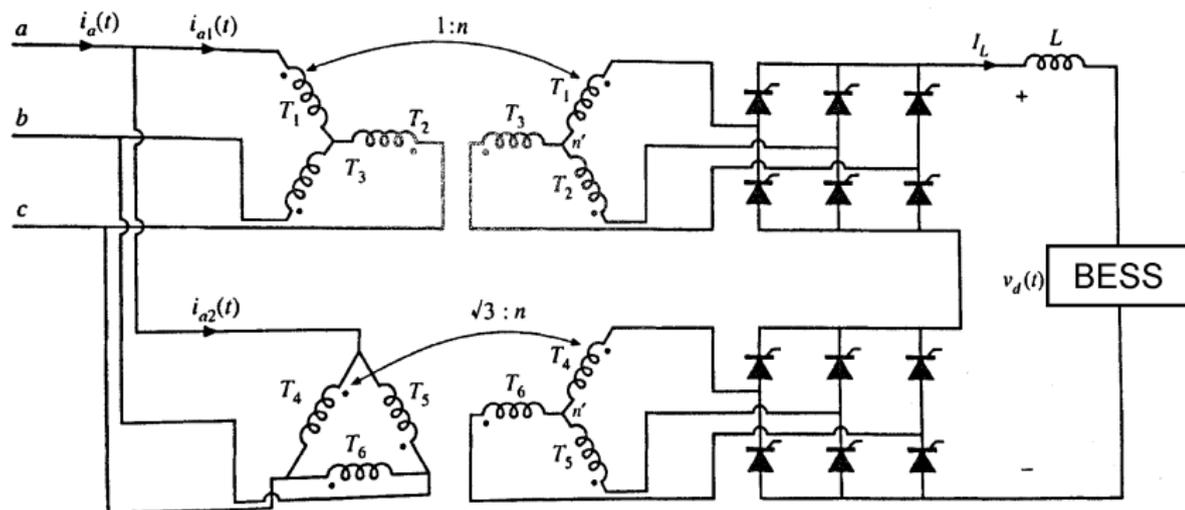

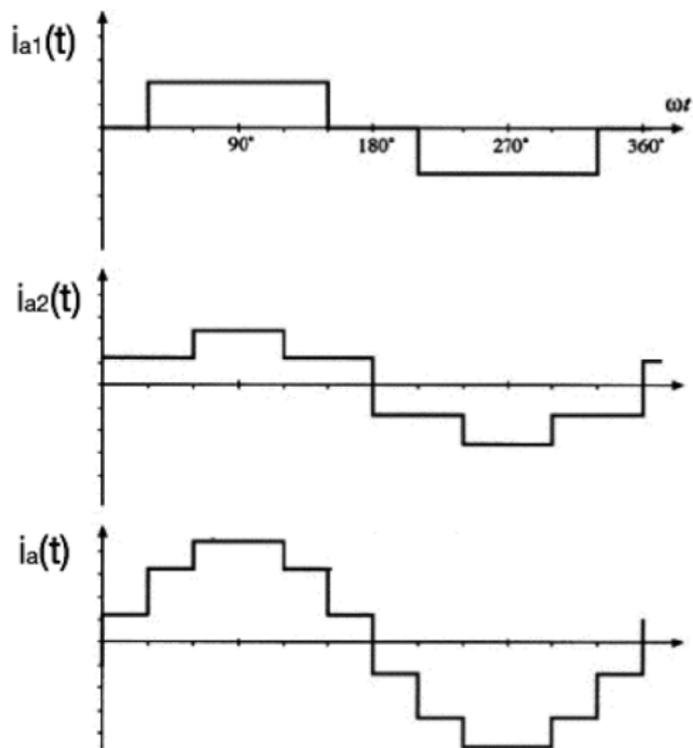The 12-pulse converter: current waveforms



Rectifier Control Strategies

- ▶ There are two possible control strategies for the 12-pulse converter:
 - ▶ P-Q modulation: allows the (joint) control of active and reactive power;
 - ▶ P modulation: reactive power supplied by the BESS is set to zero, and only active power is controlled.
- ▶ For frequency control, which requires only incremental active power variations, the **P-modulation scheme** is employed.